

$$8.11) \quad t < 0;$$

$$V_0 = 100 \text{ V}$$

$$I_0 = 5 \text{ A}$$

$$t > 0;$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \cdot 50 \cdot (25 \times 10^{-6})} = 400 \text{ rad/s}$$

$$\omega_0 = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{(160 \times 10^{-3}) \cdot (25 \times 10^{-6})}} = 500$$

$$\omega_d = \sqrt{500^2 - 400^2} = 300 \text{ rad/s}$$

$$V_0 = B_1 e^{-400t} \cos 300t + B_2 e^{-400t} \sin 300t$$

$$V_0(0) = B_1 = 100$$

$$\frac{dV_0}{dt} = -\alpha B_1 + \omega_d B_2 = \frac{1}{C} \left( -I_0 - \frac{V_0}{R} \right)$$

$$= (400) \cdot (100) + 300 B_2 = \frac{1}{25 \times 10^{-6}} \cdot \left( -5 - \frac{100}{50} \right)$$

$$= B_2 = -800$$

$$V_0 = 100 e^{-400t} \cos 300t - 800 e^{-400t} \sin 300t \quad t > 0.$$

$$8.27) \quad \omega_0 = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{(25 \times 10^{-3}) \cdot (62.5 \times 10^{-6})}} = 800 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \cdot (12.5) \cdot (62.5 \times 10^{-6})} = 640 \text{ rad/s}$$

$$\omega_d = \sqrt{800^2 - 640^2} = 480 \text{ rad/s}$$

$$I_f = 2 \text{ A}$$

$$i_L = 2 + B_1' e^{-640t} \cos 480t + B_2' e^{-640t} \sin 480t$$

$$i_L(0) = 2 + B_1' = 1$$

$$\boxed{B_1' = -1}$$




$$\frac{di_L}{dt}(0) = -a\beta_1' + \omega_d \cdot \beta_2' = \frac{V_0}{L}$$

$$\beta_2' = 2.83$$

$$-640(-1) + 480\beta_2' = \frac{50}{25 \times 10^{-3}}$$

$$i_L(t) = 2 - e^{-640t} \cos 480t + 2.83 e^{-640t} \sin 480t \text{ A ; } t \geq 0$$

8.35)  $t \geq 0$

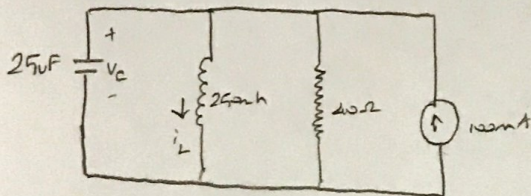

$$a = \frac{1}{2RC} = \frac{1}{2 \cdot 40 \cdot (25 \times 10^{-6})} = 500 \text{ rad/s}$$

$$\omega_0 = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{(25 \times 10^{-3}) \cdot (25 \times 10^{-6})}} = 400$$

$$a^2 > \omega_0^2$$

→ overdamped

$$s_{1,2} = -500 \pm \sqrt{500^2 - 400^2} = -200, -800$$

$$a) i_L = I_f + A_1 e^{-200t} + A_2 e^{-800t}$$

$$I_f = 100 \text{ mA}$$

$$i_L(0) = 0.1 + \underbrace{A_1 + A_2}_0 = 0.1$$

$$\frac{di_L}{dt}(0) = -200A_1 - 800A_2 = \frac{V_0}{L}$$

$$\frac{75}{0.25} = \frac{V_0}{L} = 300$$

$$A_1 = 0.9 \quad A_2 = -0.9$$

$$i_L(t) = 0.1 + 0.9 e^{-200t} - 0.9 e^{-800t} \text{ A}$$


$$b) V_c(t) = V_L(t)$$

$$L \cdot \frac{di_L}{dt} = 0.25 \cdot (-100 e^{-200t} + 400 e^{-800t})$$

$$= -25 e^{-200t} + 100 e^{-800t} \text{ V } \quad t \geq 0$$



847)  $t < 0$

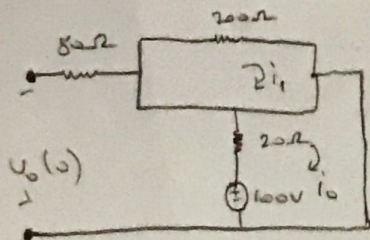


$$\begin{aligned} 500i_1 - 100i_o &= 0 \\ -100i_1 + 120i_o &= 100 \end{aligned}$$

$$i_1 = 0.2 \text{ A}$$

$$i_o = 1 \text{ A}$$

$$V_o = -100 + \underbrace{20}_{20}i_o + \underbrace{100}_{20}i_1 = -60 \text{ V}$$

$t > 0$  ;

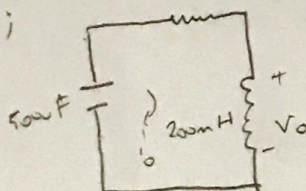

$$\alpha = \frac{R}{2L} = \frac{200}{2(0.2)} = 500$$

$$\alpha^2 > \omega_0^2$$

Over damped

$$\omega_0 = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{(0.2)(36.25 \times 10^{-6})}} = 400$$

$$s_{1,2} = -100 \pm \sqrt{500^2 - 400^2} = -200, -800 \text{ rad/s}$$

$$i_o = A_1 e^{-200t} + A_2 e^{-800t}$$

$$i_o(0) = A_1 + A_2 = 1$$

$$\frac{di_o}{dt}(0) = -200A_1 - 800A_2 = \frac{1}{L}(-V_o - RI_o) = -700$$


$$A_1 = 166.67 \text{ mA}$$

$$A_2 = 833.33 \text{ mA}$$

$t > 0$



8.54)  $t < 0$  :

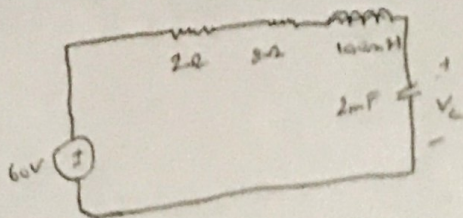

$$\alpha = \frac{R}{2L} = \frac{10}{2 \cdot (0.1H)} = 50 \text{ rad/s}$$

$$\omega_0 > \alpha$$

underdamped

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{(0.1)(2 \times 10^{-3})} = 5000$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -50 \pm j40$$

$$V_c = 60 + B_1' e^{-50t} \cos 40t + B_2' e^{-50t} \sin 40t = -90$$

$$B_1' = -150$$


$$C \frac{dV_c}{dt}(0) = -5$$

$$\frac{dV_c}{dt}(0) = \frac{-5}{2 \times 10^{-3}} = -2500$$

$$\frac{dV_c}{dt}(0) = -50 B_1' + 50 B_2' = -2500 \quad B_2' = -200$$

$$V_c = 60 - 150 e^{-50t} \cos 40t - 200 e^{-50t} \sin 40t \text{ V}, \quad t \geq 0$$

8.32)

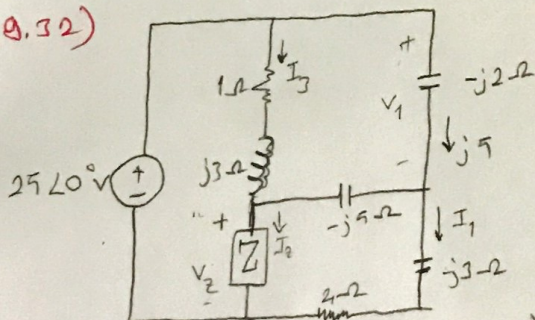

$$V_1 = j5(-j2) = 10V$$

$$-25 + 10 + (4-j3)I_1 = 0$$

$$I_1 = \frac{15}{4-j3} = 2.4 + j1.8A$$

$$I_b = I_1 - j5 = (2.4 + j1.8) - j5 = 2.4 - j3.2A$$

$$V_2 = j5I_2 + (4-j3)I_1 = j5(2.4 - j3.2) +$$

$$(4-j3)(2.4 + j1.8) = -1 - j12V$$

$$-25 + (1+j3)I_3 + (-1-j12) = 0$$

$$I_3 = 6.2 - j6.6A$$

$$I_2 = I_3 - I_b = 3.8 - j3.4A$$

$$Z = \frac{V_2}{I_2} = 1.42 - j1.88\Omega$$

(3)



9.4f) First step:  $(0.12/0^\circ)(250) = 30/0^\circ V$

Second step:  $250 - j400 + j150 = 250 - j250 \Omega$


$\frac{30/0^\circ}{250 - j250} = 60 - j60 mA$

Third Step: <sup>to find</sup>


$(250 - j250) \parallel 500 = 200 - j100 \Omega$

$(200 - j100) \cdot (0.06 - j0.06) = 18 - j6 V$


Step 1

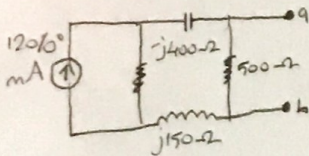


Step 3

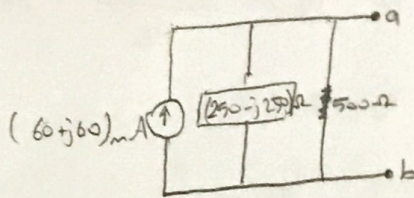


Step 2

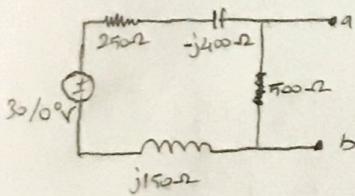

Step 4

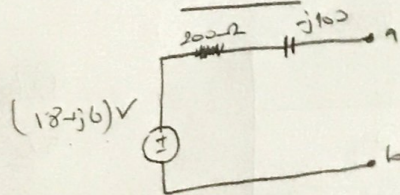

9.4b)

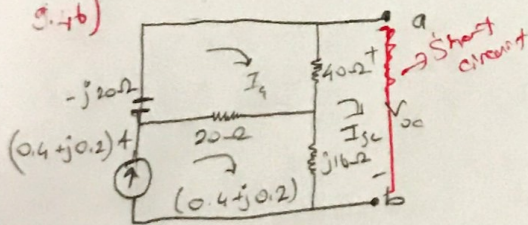

Open Circuit

$$-j20I_a + 40I_a + 20(I_a - 0.4 - j0.2) = 0$$

$$I_a = \frac{20 \cdot (0.4 + j0.2)}{60 - j20} = 0.1 + j0.1 A$$

$$V_{oc} = 40I_a + j16(0.4 + j0.2) = 0.8 + j10.4 V$$

Short Circuit:


$$-j20I_a + 40(I_a - I_{sc}) + 20(I_a - 0.4 - j0.2) = 0$$

$$40(I_{sc} - I_a) + j16(I_{sc} - 0.4 - j0.2) = 0$$

$$I_{sc} = 0.3 + j0.5 A, \quad Z_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{0.8 + j10.4}{0.3 + j0.5} = 16 + j8 \Omega$$



9.55)

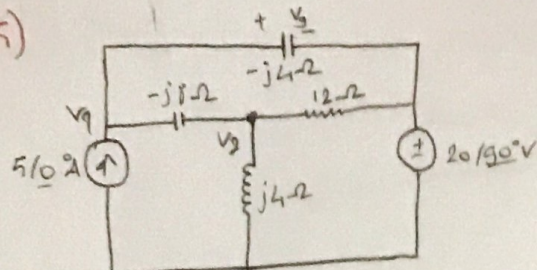

$$V_1 = -5/0^\circ + \frac{V_1 - V_2}{-j8} + \frac{V_2 - 20/90^\circ}{-j4} = 0, \quad V_2 = \frac{V_2 - V_1}{-j8} + \frac{V_2}{j4} + \frac{V_2 - 20/90^\circ}{12} = 0$$


$$V_1 \left( \frac{1}{-j8} + \frac{1}{-j4} \right) + V_2 \left( -\frac{1}{j8} \right) = 5/0^\circ + \frac{20/90^\circ}{-j4}$$

$$V_1 \left( -\frac{1}{j8} \right) + V_2 \left( \frac{1}{-j8} + \frac{1}{j4} + \frac{1}{12} \right) = \frac{20/90^\circ}{12}$$

$$V_1 = -\frac{8}{j} + j\frac{4}{3}, \quad V_2 = -8 - j4$$

$$V_g = V_1 - 20/90^\circ = -\frac{8}{j} - j\frac{56}{3} V$$

9.62)

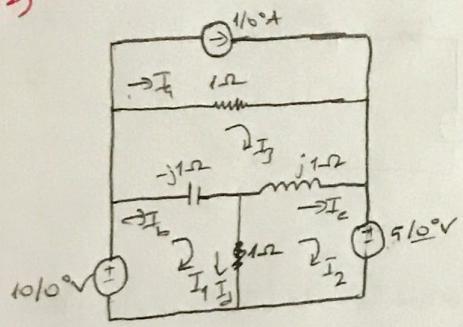

$$10/0^\circ = (1-j1)I_1 - 1I_2 + j1I_3$$

$$-5/0^\circ = -1I_1 + (1+j1)I_2 - j1I_3$$

$$j1I_1 - j1I_2 + I_3 = 1$$

$$I_1 = 11 + j10 A$$

$$I_2 = 11 + j5 A$$

$$I_3 = 6 A$$

$$I_4 = I_3 - I_1 = 5 A$$

$$I_5 = I_1 - I_3 = 5 + j10 A$$

$$I_6 = I_2 - I_3 = 5 + j5 A$$

$$I_7 = I_1 - I_2 = j5 A$$

Ersm Alin  
1801042692